



ST485ER FOR E-METER APPLICATIONS

S. Ranno**1. ABSTRACT**

This application note explains the procedure for designing the RS-485 communication lines in energy metering applications. It helps e-meter engineers to build-up their projects.

2. INTRODUCTION

Energy meters are used to monitor personal usage of electricity. In the past only one kind of e-meter was employed. This was an electromechanical device and required human employment for the periodic on-site data collection. The new frontier in energy metering is a new generation of electronic e-meters providing new features such as networked data collection, auto-diagnose and time-scheduled accounting differentiation, in order to define different energy costs on differently defined time segments. These meters provide monitoring, analysis and data storage on energy usage.

The network connection between meters allows for centralized data collection with the significant advantage that manual meter reading is no longer necessary. Moreover, it makes locating meters easier, since external accessibility (in order to get a manual reading) is unnecessary.

The network architecture can be of different types: bus, daisy chain, tree structure and so on. One of the most efficient is the bus architecture: each meter is connected to the main bus through a stub, which is kept as short as possible. The communication should be bi-directional. Each meter, in fact, needs to send data, as well as receive data from the central control, like permission to send tariff upgrades, diagnostic routines, setups, etc.

Modern communication technologies offer several choices of communication with meters. One of these methods is the use of a twisted pair cable, using RS-485 differential transmission. It offers a wide choice of transceivers available on the market, high data rates over long line lengths, high noise rejection, and a good electrical robustness, that makes it suitable in rugged environments.

3. RS-485 INTERFACES

With RS-485 two kinds of communication line can be built up: half or full duplex. A full duplex line requires four wires, and each node can simultaneously send data on two wires, while receiving from the other pair of wires. A half duplex line uses only a pair of wires for both sending and receiving, and in this case only one node at any one time can send data on the line (see figures 1 and 2). This means that two or more nodes, sending contemporaneously data to the bus, cause errors in data transmission. It is the application engineer's responsibility to choose the proper network management method, in order to avoid this problem. This choice may be constrained by the need to use a pre-defined protocol on the network,

or by the limitation of the calculated power of the network controller.

Figure 1: Rs-485 half-duplex network


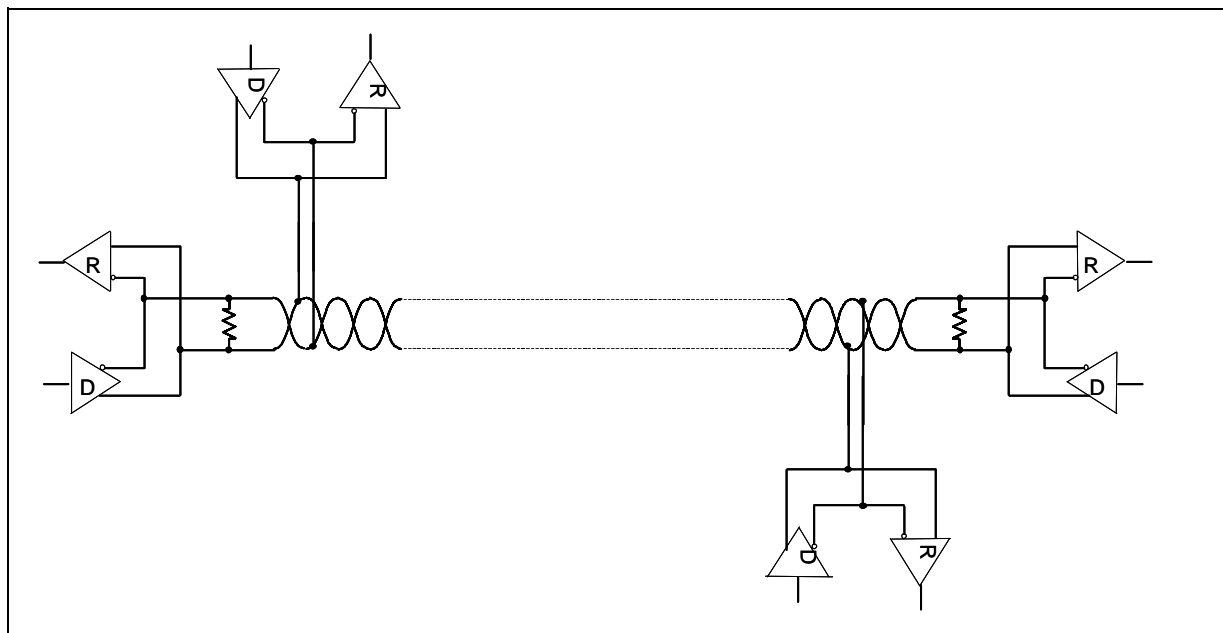


Figure 2: Rs-485 full-duplex network

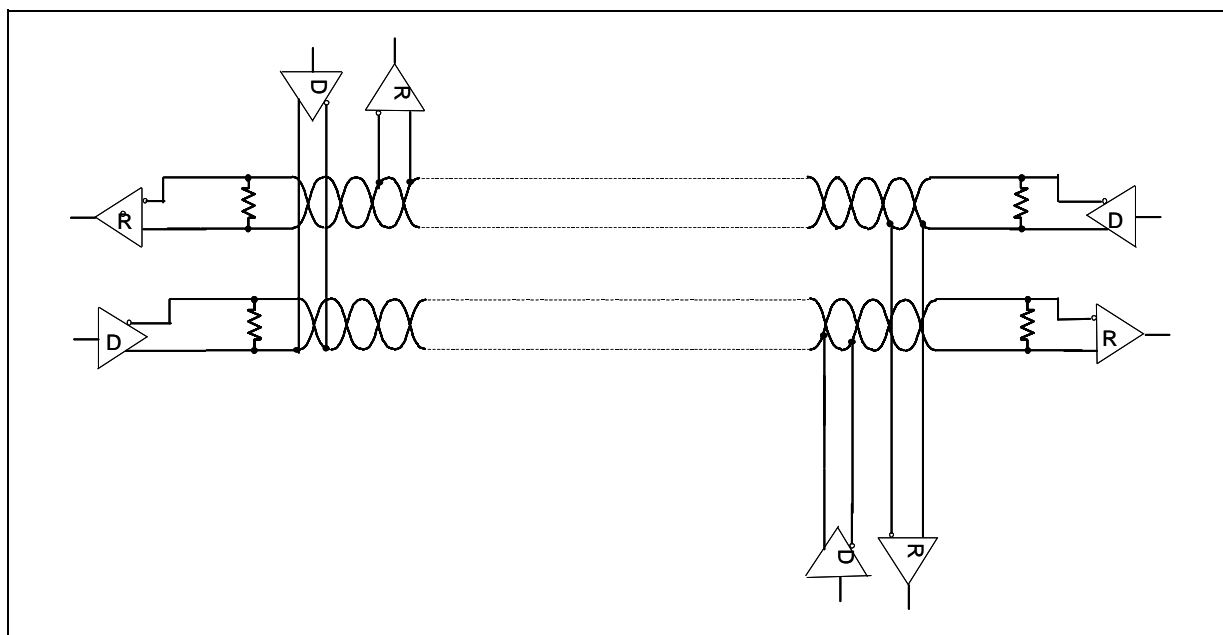

4. RS-485 ADVANTAGES

Data transmission in e-meter applications occurs in noisy environments. Meters are connected to the ac voltage, often located near industrial machinery or home appliances and the transmission line is often very long (hundreds of meters) allowing atmospheric noise to degrade signal quality.

For these reasons, RS-485 signaling is particularly relevant. Its differential drivers and receivers, in fact, reject external noise (theoretically coupled equally into both lines) with high field strength.

Project equipment employing RS-485 signaling requires the application of some rules. Differential lines must be kept close to each other, the use of a twisted pair cable is recommended and the board layout should be realized with traces of equal length for the differential signals. Impedance matching also has to be considered in order to avoid signal reflections.

5. SIGNAL LEVELS

RS-485 drivers must produce a differential output voltage of at least 1.5V into a 54ohm load (usually the lines are terminated at both ends with a 120ohm resistor; each driver seeing a $120/2=60\text{ohm}$ load, 54ohm being the worst case (10% tolerance). Receivers must detect a differential voltage as low as 200mV. This is because if a degradation of the signal occurs across the line, the communication must not be affected. However, the driver differential output voltage depends on its output current capability. If many receivers are connected to the line, the driven load seen by the driver increases, as receivers are added to the bus, requiring more current. The RS-485 standard defines a unit load (UL), which is about a 12kohm resistance over the bus voltage range interval (-7 to +12V). RS-485 drivers must generate the required output minimum voltage (1.5V) with at least 32 unit loads on a terminated bus with a 120ohm resistor on each end of the line.

The ST485ER is a half-duplex RS-485 transceiver, with a low unit load. A network provided with these 1/8 UL transceivers allows interconnection of 256 nodes, driven by means of a standard compliant driver, without overloading it.


6. BUS LENGTHS

The signal quality is evidently affected when the length of the bus increases. The most significant factor is the attenuation of the high frequency components of the signal. This produces slackening of the rising and falling edge of the signal as well as jitter and inter-symbol interference. All these factors must be taken into account when considering the cable length and signaling rate. Most e-meter applications require signaling rates below 250kbit/s. With these rates, the signal degradation is less evident for cable lengths up to 1km. The ST485ER is suitable for these signaling rates. Its driver outputs have a slew rate limitation, which reduces EMI and signal reflections on the line, allowing very low signal degradation over long distances.

7. NETWORK ISOLATION


Due to the long distance covered by the network, many factors such as ground loops, external noise, spikes, electrical storms, or common-mode voltages exceeding the maximum voltage range (-7V to +12V), can bother or, in some cases, damage the equipment connected to the TTL side of each transceiver (see figure 3).

Figure 3: Dangerous ground shifts in a common situation

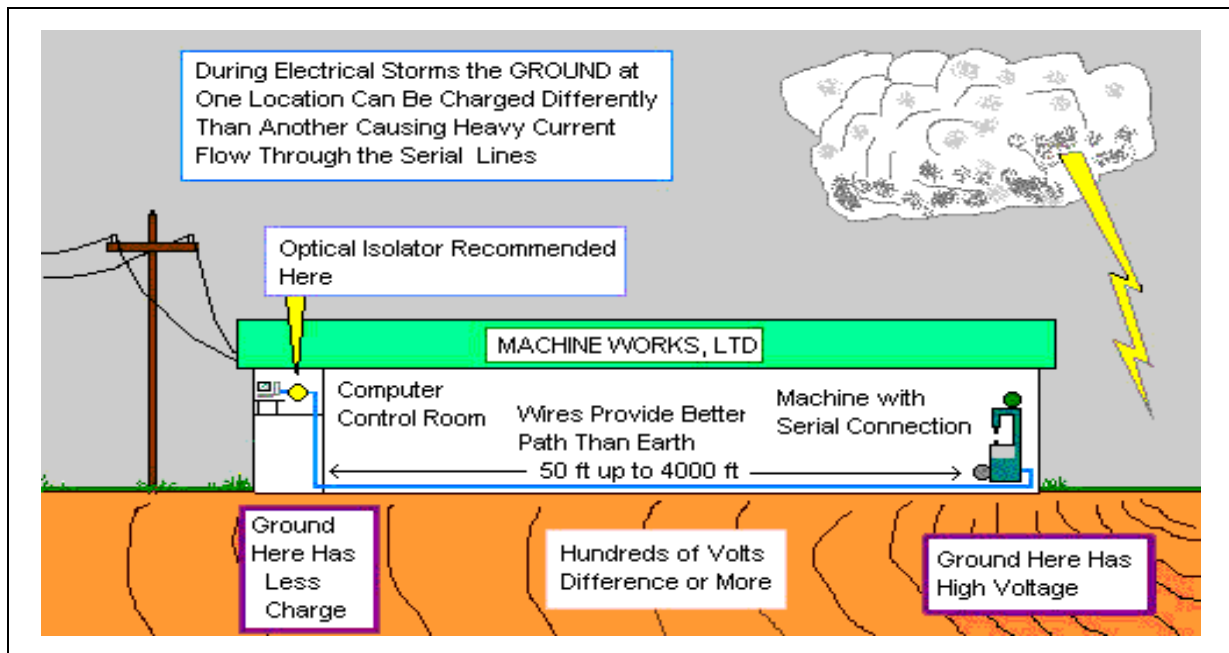

In order to avoid this, it is advisable to electrically isolate the equipment from the bus. In figure 4 an example is shown of isolated transceivers, requiring the use of optocouplers at any single-ended (TTL input/output) terminal. Note that two isolated power supplies are employed: one for the transceivers and the related sides of the optocouplers connected to them (VBUS), the other one for the equipment and the other sides of the optocouplers (VTTL). These two supplies should be isolated from each other, and derived from different power generators or transformer windings.

Figure 4: Rs-485 terminal node with optocouplers

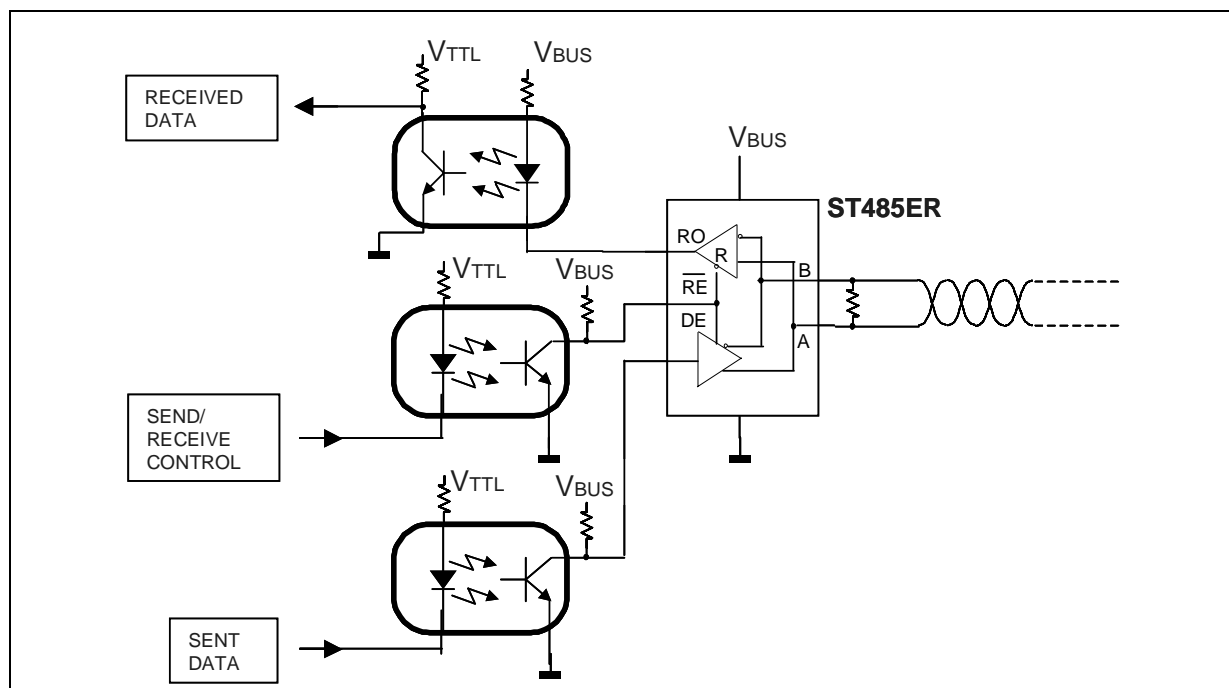

The choice of proper optocouplers should be based on rise and fall times, which are related to the signaling rate. The RS-485 requirements for the signal quality are that the rise (or fall) time should not exceed 30% of the bit time (reciprocal of the signaling rate). For a signaling rate of 250kbit/s, the maximum rise or fall time of the optocouplers is:

$$0.3 * (\text{bit time}) = 0.3(1/250\text{kbps}) = 1.2\mu\text{sec}$$


Therefore, an optocoupler with rise/fall times faster than 1.2μsec is required. The biasing resistors should be selected taking into account the current characteristics of the optocouplers, and the threshold voltages of the transceiver input pins, in order to ensure a reliable driving of the transceiver.

8. FAILSAFE BIASING

In an RS-485 network, a driver is always active on the line. Therefore, each receiver has differential input voltages, which exceed the 200mV minimum threshold voltage, ensuring a known logic state at its output. When a receiver is disconnected from the bus (receiver inputs floating), its output assumes an undetermined logic state. The ST485ER has an internal failsafe feature, which avoids this problem. A weak internal biasing ensures a receiver differential voltage higher than 200mV, and therefore a valid logic state at its output under floating inputs conditions.

A different situation occurs when there are no active drivers on the network (idle-bus). In this case, the receivers are connected to the bus and to the termination resistors. The termination resistors decrease the differential voltage near 0V, and the internal failsafe is not able to ensure a proper voltage level. Some transmission protocol (for example the UART protocol) requires a high logic state of the bus when in idle state. In order to solve this problem, two biasing resistors should be applied to the two line wires, giving a proper biasing of the line (see also the application note "failsafe biasing for ST485"). In a terminated bus with a 120-ohm termination resistor at each end, the equivalent resistance is 60ohm ($120\text{ohm}/2$). In order to produce a differential voltage at its leads higher than 200mV, a current of 4mA should flow into it. In order to guarantee this current without unmatching the characteristic impedance of the line, 500/600ohm resistors should be used(see the figure 5).

Figure 5: External failsafe and line DC termination

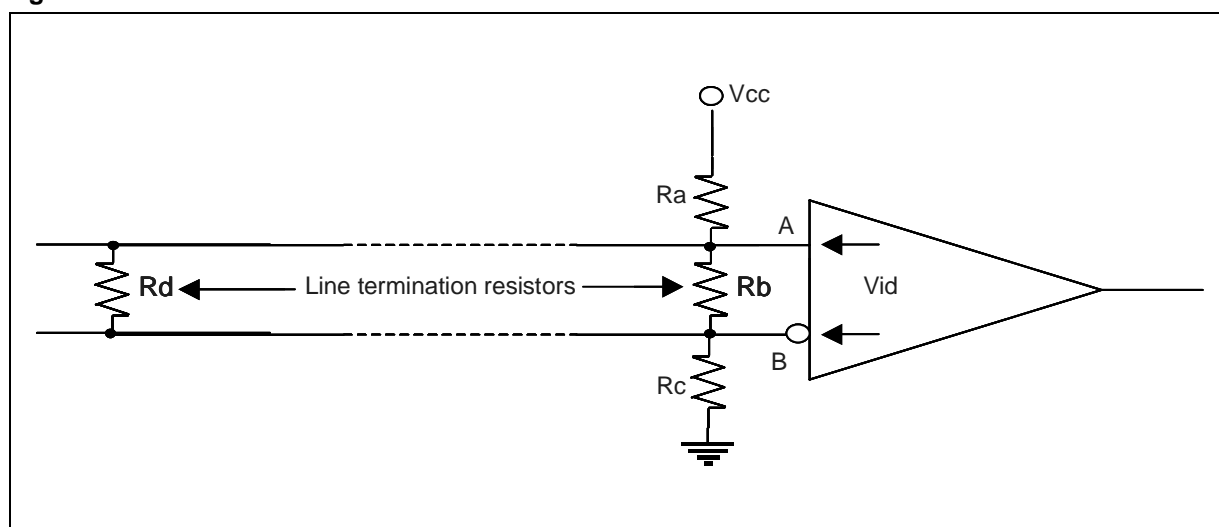


The external failsafe circuitry should be placed at one end of the bus or at each end of it, using, in this case, twice the value calculated for one biasing circuit (1K/1.2Kohm) and, of course, it should not be disconnected for any reason.

The external failsafe circuitry draws current; therefore it loads the driver outputs. This extra-load should be taken in account defining the maximum number of transceivers allowed on the bus. The equivalent load of the failsafe circuitry, seen by the active driver is, for $R_a = R_c = 500\Omega$, 24UL. Since the maximum allowed on the bus is 32UL, the available unit loads should be $32UL - 24UL = 8UL$. Using the ST485ER (1/8UL per transceiver) the maximum number of transceivers should be: $8UL / (1/8UL \text{ per transceiver}) = 64$ transceivers.

9. TRANSIENT VOLTAGE SUPPRESSION

Transient voltage surges are generated generally by inductive load switching, for example, the equipment starts and stops, lightning strikes, etc. The standard IEC 61000-4-5 Immunity Test describes a method to test circuits with a waveform simulating these conditions (see figure 6).


Figure 6: IEC 61000-4-5 Transient Voltage Test V and I Waveforms

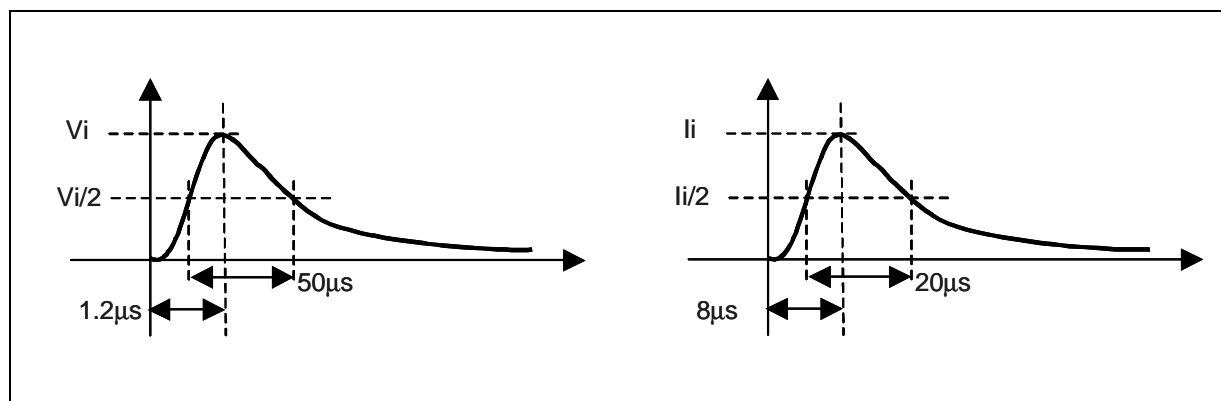

Surge voltages inducted on both differential lines do not affect the entire system operation, if the bus is isolated, and the ground voltage shift generated does not exceed the maximum ratings. However, the use of additional transient voltage suppressors (TVS) is advisable, in order to protect against surges in case of miswiring, incorrect grounding and other fault conditions. ST offers a wide range of TVS. Visit the site: <http://eu.st.com/stonline/discretes/index.shtml>. The selection criteria are the stand-off voltage (VRM), the clamping voltage (VCL) and the peak power dissipation (PD). The stand-off voltage must not exceed the operating common mode voltage range (-7 to +12V), in order to avoid clamping during the normal operation, while the clamping voltage must be low enough to hold the line voltage with no damage to the protected circuits. The peak power dissipation is the product of the clamping voltage and the peak current that can be managed by the TVS without being harmed. One TVS suitable for a RS-485 network is the ST's SMA12CA. It has:

$$V_{RM} = \pm 12V; V_{CL} = 19.9V @ I_{PEAK} = 20A; P_D = 400W$$

Figure 7: Usage of the Transient voltage suppressors in the RS-485 network

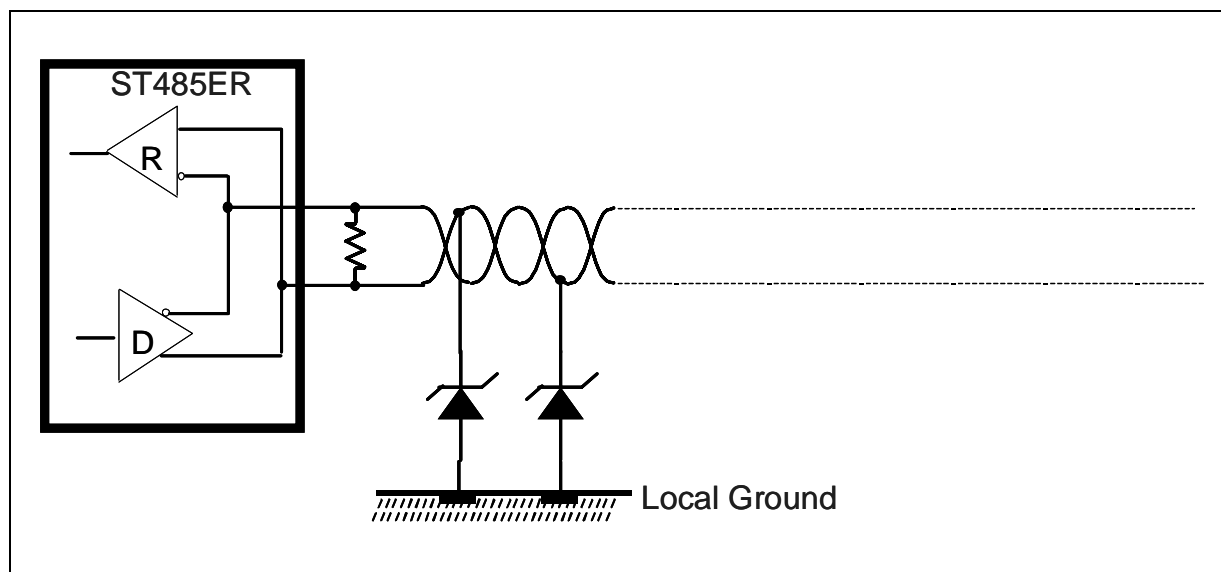

10. ESD PROTECTION

Some usual situation like handling, connection and maintenance, can create electro-static discharges (ESD), which can damage the related devices. Use of transceivers with high ESD immunity in e-meter applications is recommended. In order to evaluate ESD immunity, two standards are largely employed at the time: the JEDEC standard (Human Body Model), which simulates the ESD of a human body contacting the device, and the ISO standard (IEC 61000-4-2), which simulates the ESD of a human body handling a tool (screwdriver, or a metallic connector, etc.), approaching (Air Discharge) or contacting (Contact Discharge) the device. The IEC 61036 standard requires the device should be immune to contact discharges (ISO IEC 61000-4-2) of 8kV, while the DL/T 645 standard requires meter equipments to tolerate 15kV (HBM) discharges.

The ST485ER is compliant to both these specifications.

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specification mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a registered trademark of STMicroelectronics

© 2003 STMicroelectronics - Printed in Italy - All rights reserved

STMicroelectronics GROUP OF COMPANIES

Australia - Brazil - Canada - China - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia -
Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - U.S.A.

<http://www.st.com>